

Gate 1: (AND) : $D_1 = X \cdot Q_1$

Gate 2: (OR) : $D_2 = Q_1 + Q_2$

Gate 3: (OR) : $Z = X + Q_2$

D FF: next state = Output on next clock edge

Q_1	Q_2	X	$D_1 = X \cdot Q_1$	$D_2 = Q_1 + Q_2$	$Z = X + Q_2$
0	0	0	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	0	1	1

$D_1, D_2 = \text{next state name}$

State	X	$D_1, D_2 \text{ (next)}$	State Name	Z
A (00)	0	01	B	0
A (00)	1	11	D	1
B (01)	0	00	A	1
B (01)	1	10	C	1
C (10)	0	01	B	0
C (10)	1	01	B	1
D (11)	0	01	B	1
D (11)	1	01	B	1

Transition Diagram

$A - x=0/z=0 \rightarrow B$

$A - x=1/z=1 \rightarrow D$

$B - x=0/z=1 \rightarrow A$

$B - x=1/z=1 \rightarrow C$

$C - x=0/z=0 \rightarrow B$

$C - x=1/z=1 \rightarrow B$

$D - x=0/z=1 \rightarrow B$

$D - x=1/z=1 \rightarrow B$